RENESAS

HD74LS145

# BCD-to-Decimal Decoder / Driver (with 15 V outputs)

REJ03D0436-0300 Rev.3.00 Jul.13.2005

This BCD-to-decimal decoder / driver consists of eight inverters and ten four-input NAND gates. The inverters are connected in pairs to make BCD input data available for decoding by the NAND gates. Full decoding of valid BCD input logic ensures that all outputs remain off for all invalid binary input conditions. This decoder features high-performance, n-p-n output transistors designed for use as indicator / relay drivers or as open-collector logic-circuit drivers.


### Features

• Ordering Information

Part Name	Package Type	Package Code (Previous Code)	Package Abbreviation	Taping Abbreviation (Quantity)	
HD74LS145P	DILP-16 pin	PRDP0016AE-B (DP-16FV)	Ρ	—	
HD74LS145FPEL	SOP-16 pin (JEITA)	PRSP0016DH-B (FP-16DAV)	FP	EL (2,000 pcs/reel)	

Note: Please consult the sales office for the above package availability.

### **Pin Arrangement**

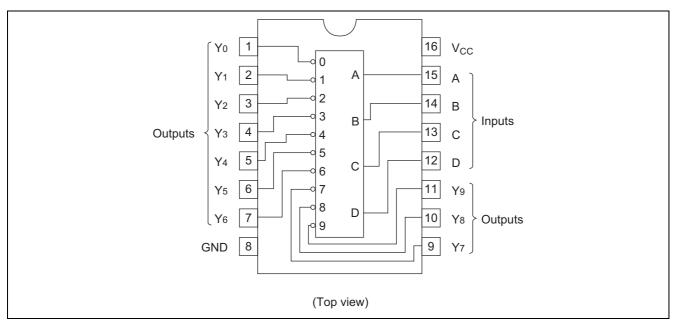




## **Function Table**

No.					Outputs									
NO.	D	С	В	Α	0	1	2	3	4	5	6	7	8	9
0	L	L	L	L	L	Н	Н	Н	Н	Н	Н	Н	Н	Н
1	L	L	L	Н	Н	L	Н	Н	Н	Н	Н	Н	Н	Н
2	L	L	Н	L	Н	Н	L	Н	Н	Н	Н	Н	Н	Н
3	L	L	Н	Н	Н	Н	Н	L	Н	Н	Н	Н	Н	Н
4	L	Н	L	L	Н	Н	Н	Н	L	Н	Н	Н	Н	Н
5	L	Н	L	Н	Н	Н	Н	Н	Н	L	Н	Н	Н	Н
6	L	Н	Н	L	Н	Н	Н	Н	Н	Н	L	Н	Н	Н
7	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	L	Н	Н
8	Н	L	L	L	Н	Н	Н	Н	Н	Н	Н	Н	L	Н
9	Н	L	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	L
	Н	L	Н	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
	Н	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
Invalid	Н	Н	L	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
invaliu	Н	Н	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
	Н	Н	Н	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н

### **Block Diagram**

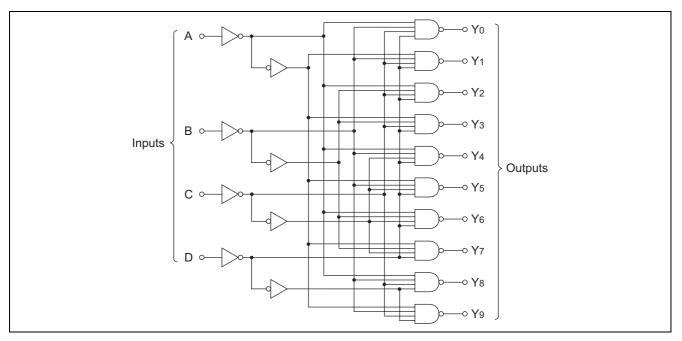

### **Absolute Maximum Ratings**

ltem	Symbol	Ratings	Unit
Supply voltage	V <sub>CC</sub>	7	V
Input voltage	V <sub>IN</sub>	7	V
Power dissipation	P <sub>T</sub>	400	mW
Storage temperature	Tstg	–65 to +150	°C

Note: Voltage value, unless otherwise noted, are with respect to network ground terminal.



### **Recommended Operating Conditions**

Item	Symbol	Min	Тур	Max	Unit
Supply voltage	V <sub>CC</sub>	4.75	5.00	5.25	V
Off-state output voltage	V <sub>O(off)</sub>	—	—	15	V
Low level output current	l <sub>OL</sub>	—	—	80	mA
Operating temperature	Topr	-20	25	75	°C

## **Electrical Characteristics**

 $(Ta = -20 \text{ to } +75 \ ^{\circ}\text{C})$ 

ltem	Symbol	min.	typ.*	max.	Unit	Condition
Input voltage	VIH	2.0	_	—	V	
Input voltage	VIL	_	_	0.8	V	
Off-state output current	I <sub>O(off)</sub>	_		250	μA	$\label{eq:VCC} \begin{array}{l} V_{CC} = 4.75 \ \text{V}, \ V_{IH} = 2 \ \text{V}, \ V_{IL} = 0.8 \ \text{V}, \\ V_{O(off)} = 15 \ \text{V} \end{array}$
	V <sub>O(on)</sub>	_		0.4	V	$I_{OL} = 12 \text{ mA}$ $V_{CC} = 4.75 \text{ V}, \text{ V}_{IH} = 2 \text{ V},$
On-state output voltage		—	-	0.5		$I_{OL} = 24 \text{ mA}$ $V_{CC} = 4.73 \text{ V}, \text{ V}_{IH} = 2 \text{ V},$ $V_{II} = 0.8 \text{ V}$
Voltage		—		3.0		I <sub>OL</sub> = 80 mA
	IIH	—		20	μΑ	$V_{CC} = 5.25 \text{ V}, \text{ V}_{I} = 2.7 \text{ V}$
Input current	IIL	—		-0.4	mA	$V_{CC} = 5.25 \text{ V}, \text{ V}_{I} = 0.4 \text{ V}$
	I <sub>I</sub>	—		0.1	mA	$V_{CC} = 5.25 \text{ V}, \text{ V}_{I} = 7 \text{ V}$
Supply current**	Icc		7	13	mA	V <sub>CC</sub> = 5.25 V
Input clamp voltage	VIK	—		-1.5	V	$V_{CC} = 4.75 \text{ V}, I_{IN} = -18 \text{ mA}$

Notes: \*  $V_{CC} = 5 V$ , Ta = 25°C

 $^{\star\star}$  I\_{CC} is measured with all outputs open and all inputs grounded.

### **Switching Characteristics**


 $(V_{CC} = 5 V, Ta = 25^{\circ}C)$ 

ltem	Symbol	min.	typ.	max.	Unit	Condition	
Propagation delay time	t <sub>PLH</sub>	-	—	50	ns	$C_{L} = 45 \text{ pF}, R_{L} = 665 \Omega$	
Fropagation delay time	t <sub>PHL</sub>		—	50	115	$G_L = 45  \text{pr},  \text{R}_L = 665  \Omega$	




## **Testing Method**

#### **Test Circuit**

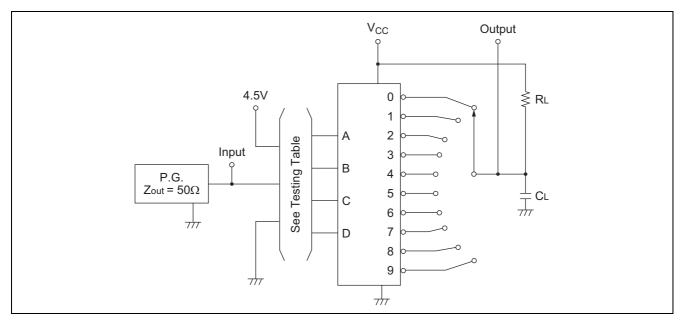


#### Waveform

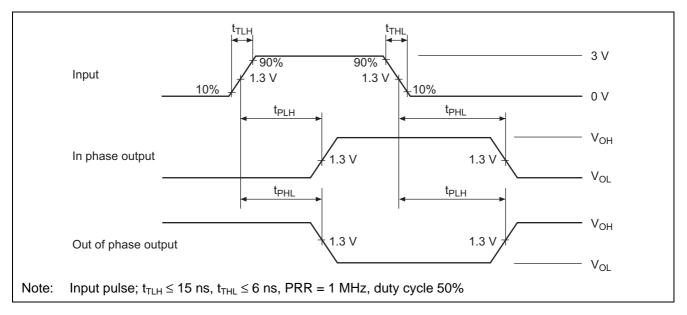



### **Package Dimensions**

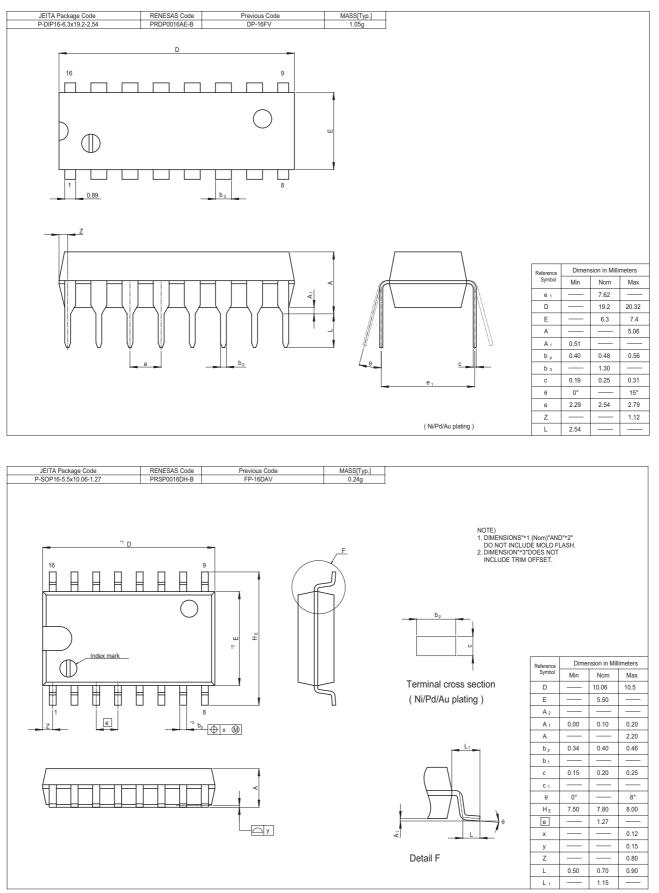



## Renesas Technology Corp. sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

Keep safety first in your circuit designs! 1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

#### Notes regarding these materials

- Notes regarding these materials
   These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.
   Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
   All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. vithout notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information before purchasing a product listed herein.
   The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors. Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (http://www.renesas.com).
   When using any or all of the information contained in these materials. including product data, diagrams, charts, programs, and algorithms, please be sure to

- Nome page (ntp://www.renesas.com).
  4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
  5. Renesas Technology Corp. semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
- use. 6. The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials. 7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination. Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited. 8. Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.



#### **RENESAS SALES OFFICES**

Refer to "http://www.renesas.com/en/network" for the latest and detailed information.

Renesas Technology America, Inc. 450 Holger Way, San Jose, CA 95134-1368, U.S.A Tel: <1> (408) 382-7500, Fax: <1> (408) 382-7501

Renesas Technology Europe Limited Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K. Tel: <44> (1628) 585-100, Fax: <44> (1628) 585-900

Renesas Technology Hong Kong Ltd.

7th Floor, North Tower, World Finance Centre, Harbour City, 1 Canton Road, Tsimshatsui, Kowloon, Hong Kong Tel: <852> 2265-6688, Fax: <852> 2730-6071

Renesas Technology Taiwan Co., Ltd. 10th Floor, No.99, Fushing North Road, Taipei, Taiwan Tel: <886> (2) 2715-2888, Fax: <886> (2) 2713-2999

Renesas Technology (Shanghai) Co., Ltd. Unit2607 Ruijing Building, No.205 Maoming Road (S), Shanghai 200020, China Tel: <86> (21) 6472-1001, Fax: <86> (21) 6415-2952

#### Renesas Technology Singapore Pte. Ltd.

1 Harbour Front Avenue, #06-10, Keppel Bay Tower, Singapore 098632 Tel: <65> 6213-0200, Fax: <65> 6278-8001

Renesas Technology Korea Co., Ltd. Kukje Center Bldg. 18th Fl., 191, 2-ka, Hangang-ro, Yongsan-ku, Seoul 140-702, Korea Tel: <82> 2-796-3115, Fax: <82> 2-796-2145

#### Renesas Technology Malaysia Sdn. Bhd.

Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No.18, Jalan Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia Tel: <603> 7955-9390, Fax: <603> 7955-9510

© 2005. Renesas Technology Corp., All rights reserved. Printed in Japan. Colophon .3.0

http://www.renesas.com